

# EE23BTECH11217 - Prajwal M\*

## EXERCISE 9.1

The given figure shows a series LCR circuit connected to a sinusoidal 230 V source.

$L = 5.0 \text{ H}$ ,  $C = 80 \mu\text{F}$ ,  $R = 40 \Omega$ .

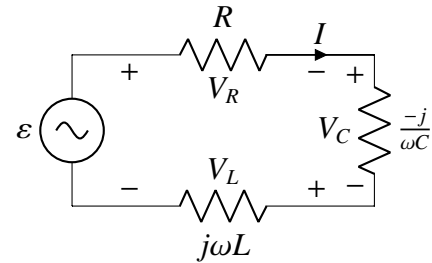
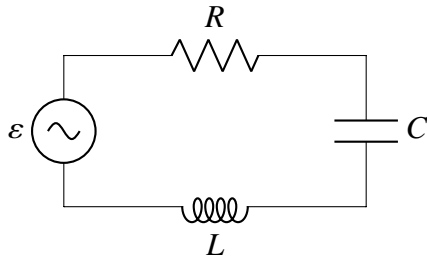


Fig. 3. circuit diagram

2)

- 1) Determine the source frequency which drives the circuit in resonance.
- 2) Obtain the impedance of the circuit at the resonating frequency.
- 3) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.

$$Z_{res} = R = 40\Omega \quad (4)$$

Solution:

Paramater	Description	Value
$\varepsilon$	Voltage power supply	$Re\{230\sqrt{2}e^{j\omega t}\} \text{ V}$
$L$	Inductance	$5.0 \text{ H}$
$C$	Capacitance	$80 \mu\text{F}$
$R$	Resistance	$40 \Omega$
$\frac{\omega}{2\pi}$	Frequency of voltage source	?
$Z$	Impedance of circuit	?
$V_R$	Potential drop across Resistor	?
$V_C$	Potential drop across Capacitor	?
$V_L$	Potential drop across Inductor	?

TABLE 3  
PARAMETER DESCRIPTION

1) from Fig. 3,

$$Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \quad (1)$$

$$\min(|Z|) = R \text{ at } \omega = \frac{1}{\sqrt{LC}} \quad (2)$$

$$f_{res} = \frac{\omega_{res}}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 7.958 \text{ Hz} \quad (3)$$

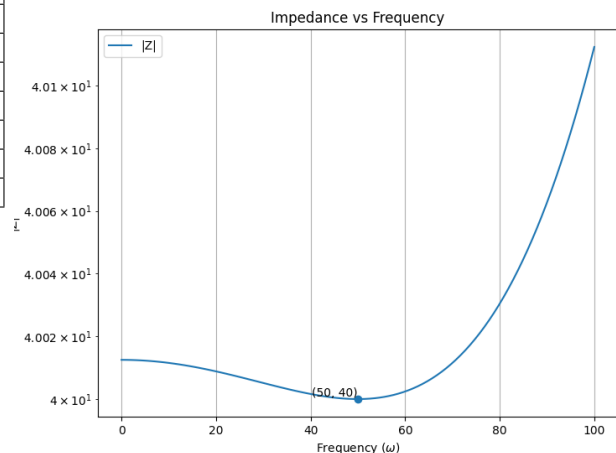


Fig. 2. Impedance vs frequency

3)

$$I_{res} = \frac{\varepsilon}{Z_{res}} \quad (5)$$

$$V_R = Re \{RI_{res}\} \quad (6)$$

$$= Re \left\{ R \frac{\varepsilon}{Z_{res}} \right\} \quad \{\text{using (5)}\} \quad (7)$$

$$= Re \{325.28e^{j50t}\} \quad (8)$$

$$= 325.28 \cos(50t) \quad (9)$$

$$V_C = Re \left\{ \frac{-j}{\omega_{res}C} I_{res} \right\} \quad (10)$$

$$= Re \left\{ \frac{-j}{\omega_{res}C} \frac{\varepsilon}{Z_{res}} \right\} \quad \{\text{using (5)}\} \quad (11)$$

$$= Re \left\{ 2032.93e^{j(50t - \frac{\pi}{2})} \right\} \quad (12)$$

$$= 2031.93 \sin(50t) \quad (13)$$

$$V_L = Re \{j\omega_{res}LI_{res}\} \quad (14)$$

$$= Re \left\{ j\omega_{res}L \frac{\varepsilon}{Z_{res}} \right\} \quad \{\text{using (5)}\} \quad (15)$$

$$= Re \left\{ 2032.93e^{j(50t + \frac{\pi}{2})} \right\} \quad (16)$$

$$= -2031.93 \sin(50t) \quad (17)$$

from (13) and (17), voltage across LC combination is  $V_C + V_L = 0V$

Paramater	Description	Value
$f_{res}$	resonant source frequency	7.958Hz
$Z_{res}$	resonant impedance	40Ω
$rms(V_R)$	rms value of $V_R$	230V
$rms(V_C)$	rms value of $V_C$	1437.5V
$rms(V_L)$	rms value of $V_L$	1437.5V

TABLE 3  
SOLUTION VALUES

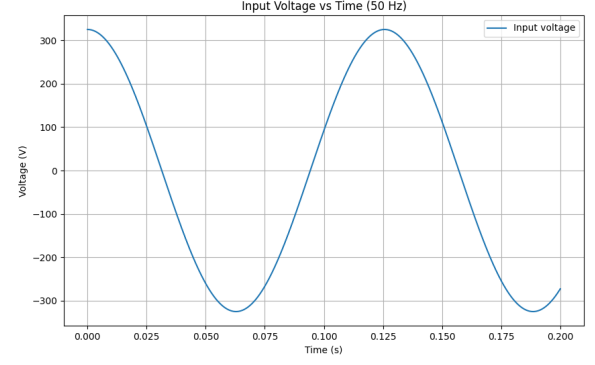


Fig. 3. Input voltage

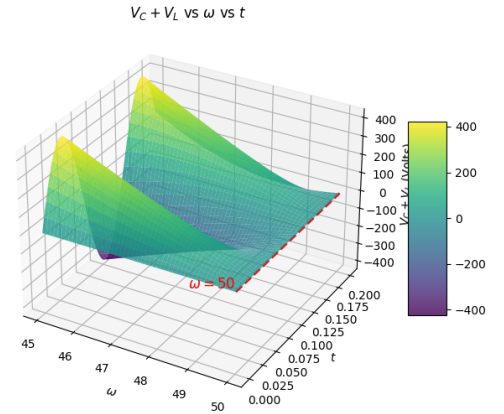


Fig. 3. Voltage across LC combination