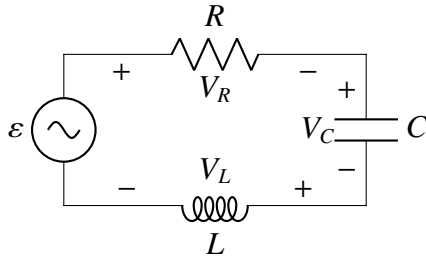


EE23BTECH11217 - Prajwal M*

EXERCISE 9.1

The given figure shows a series LCR circuit connected to a variable frequency 230 V source.
 $L = 5.0 \text{ H}$, $C = 80 \mu\text{F}$, $R = 40 \Omega$.



- 1) Determine the source frequency which drives the circuit in resonance.
- 2) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- 3) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.

Solution:

Paramater	Description	Value
L	Inductance	5.0 H
C	Capacitance	$80 \mu\text{F}$
R	Resistance	40Ω
ω_{res}	resonance frequency	50 rad/s
Z_{res}	Resonance impedance	40Ω
I_{res}	Amplitude of current at resonance	8.1 A
V_R	Potential drop across Resistor	230 V
V_L	Potential drop across Resistor	1437.5 V
V_C	Potential drop across Resistor	1437.5 V
V_{LC}	Potential drop across LC combination	0 V

TABLE 3
PARAMETER DESCRIPTION

1)

$$\omega_{\text{res}} = \frac{1}{\sqrt{LC}} \quad (1)$$

$$\omega_{\text{res}} = \frac{1}{\sqrt{(5.0 \text{ H})(80 \times 10^{-6} \text{ F})}} \quad (2)$$

$$\omega_{\text{res}} \approx 50 \text{ rad/s} \quad (3)$$

(4)

2)

$$Z_{\text{res}} = R = 40 \Omega \quad (5)$$

$$I_{\text{res}} = \frac{\sqrt{2}\epsilon}{Z_{\text{res}}} \quad (6)$$

$$= \frac{\sqrt{2}(230)}{40} \quad (7)$$

$$= 8.1 \text{ A} \quad (8)$$

3)

$$I_{\text{rms}} = \frac{I_{\text{res}}}{\sqrt{2}} \quad (9)$$

$$= \frac{8.1}{\sqrt{2}} \quad (10)$$

$$\approx 5.75 \text{ A} \quad (11)$$

$$V_R = I_{\text{rms}}R \quad (12)$$

$$= 5.75 \text{ A} \times 40 \Omega \quad (13)$$

$$\approx 230 \text{ V} \quad (14)$$

$$V_L = I_{\text{rms}}\omega_{\text{res}}L \quad (15)$$

$$= 5.75 \text{ A} \times 50 \text{ rad/s} \times 5.0 \text{ H} \quad (16)$$

$$\approx 1437.5 \text{ V} \quad (17)$$

$$V_C = I_{\text{rms}} \frac{1}{\omega_{\text{res}}C} \quad (18)$$

$$= 5.75 \text{ A} \times \frac{1}{50 \text{ rad/s} \times 80 \times 10^{-6} \text{ F}} \quad (19)$$

$$\approx 1437.5 \text{ V} \quad (20)$$

$$V_{LC} = I_{\text{rms}}\omega_{\text{res}}L - I_{\text{rms}} \frac{1}{\omega_{\text{res}}C} \quad (21)$$

$$= V_L - V_C \quad (22)$$

$$= 1437.5 \text{ V} - 1437.5 \text{ V} = 0 \text{ V} \quad (23)$$