

## EE23BTECH11217 - Prajwal M\*

## EXERCISE 9.1

The given figure shows a series LCR circuit connected to a variable frequency 230 V source.  $L = 5.0 \text{ H}$ ,  $C = 80 \mu\text{F}$ ,  $R = 40 \Omega$ .

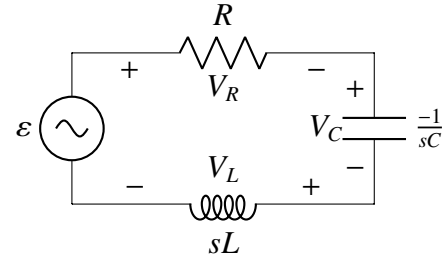
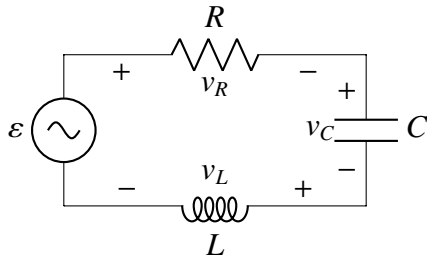


Fig. 3. s-domain circuit diagram

- 1) Determine the source frequency which drives the circuit in resonance.
- 2) Obtain the impedance of the circuit and the amplitude of current at the resonating frequency.
- 3) Determine the rms potential drops across the three elements of the circuit. Show that the potential drop across the LC combination is zero at the resonating frequency.

1)

$$V_L + V_C = 0 \quad (1)$$

$$s_{\text{res}}L - \frac{1}{s_{\text{res}}C} = 0 \quad (2)$$

$$s_{\text{res}} = \frac{1}{\sqrt{LC}} \quad (3)$$

$$s_{\text{res}} = \frac{1}{\sqrt{(5.0 \text{ H})(80 \times 10^{-6} \text{ F})}} \quad (4)$$

$$s_{\text{res}} = 50 \text{ rad/s} \quad (5)$$

Solution:

Paramater	Description	Value
$\varepsilon$	Voltage power supply	230 V
L	Inductance	5.0 H
C	Capacitance	80 $\mu\text{F}$
R	Resistance	40 $\Omega$
$s_{\text{res}}$	resonance frequency	?
$Z_{\text{res}}$	Resonance impedance	?
$I_{\text{res}}$	Amplitude of current at resonance	?
$V_R$	Potential drop across Resistor	?
$V_L$	Potential drop across Resistor	?
$V_C$	Potential drop across Resistor	?
$V_{LC}$	Potential drop across LC combination	?

TABLE 3  
PARAMETER DESCRIPTION

2)

$$Z_{\text{res}} = R = 40 \Omega \quad (6)$$

$$I_{\text{res}} = \frac{\sqrt{2}\varepsilon}{Z_{\text{res}}} \quad (7)$$

$$= \frac{\sqrt{2}(230)}{40} \quad (8)$$

$$= 8.1 \text{ A} \quad (9)$$

3)

$$I_{\text{rms}} = \frac{I_{\text{res}}}{\sqrt{2}} \quad (10)$$

$$= \frac{8.1}{\sqrt{2}} \quad (11)$$

$$\approx 5.75 \text{ A} \quad (12)$$

$$V_R = I_{\text{rms}} R \quad (13)$$

$$= 5.75 \text{ A} \times 40 \, \Omega \quad (14)$$

$$\approx 230 \text{ V} \quad (15)$$

$$V_L = I_{\text{rms}} s_{\text{res}} L \quad (16)$$

$$= 5.75 \text{ A} \times 50 \text{ rad/s} \times 5.0 \text{ H} \quad (17)$$

$$\approx 1437.5 \text{ V} \quad (18)$$

$$V_C = I_{\text{rms}} \frac{-1}{s_{\text{res}} C} \quad (19)$$

$$= 5.75 \text{ A} \times \frac{-1}{50 \text{ rad/s} \times 80 \times 10^{-6} \text{ F}} \quad (20)$$

$$\approx -1437.5 \text{ V} \quad (21)$$

$$V_{LC} = I_{\text{rms}} s_{\text{res}} L - I_{\text{rms}} \frac{1}{s_{\text{res}} C} \quad (22)$$

$$= V_L + V_C \quad (23)$$

$$= 1437.5 \text{ V} - 1437.5 \text{ V} = 0 \text{ V} \quad (24)$$